

1. Sizing a chain of inverters to drive a large capacitive load:

A minimum size inverter has $W/L = 0.375 / 0.25$ for both the NMOS and PMOS using the example process of the text. A signal from this inverter must drive a 20pF output pin with a delay time, t_p , of less than 3ns. Design an inverter chain with a minimum number of inverters to meet this specification. Do not assume that $\gamma = 1$. Use capacitance and resistance values from the solution to problem 1 of HW 3.

- Calculate the average value of C_{int} .
- Calculate γ .
- Calculate t_{p0} .
- Determine the number of inverters N .
- What are the gate widths of each inverter in the chain?

2. Static CMOS AOI logic:

- Draw the transistor implementation of a 3 input NAND gate.
- Draw the transistor implementation of a 3 input NOR gate.
- Explain why one gate is preferable to the other in this logic style.

3. Design a static CMOS AOI logic gate:

- Draw the static CMOS (AOI) implementation of $Y = \overline{A(B+CD)} + \overline{E}$ such that capacitance is minimized at the output.
- Calculate the worst case pull up and pull down times for all minimum size transistors ($W/L = 0.375 / 0.25$) assuming a 50 fF load and ignoring all other capacitances.


4. Design and compare static CMOS AOI logic versus transmission gate logic:

An XOR gate can be constructed using static CMOS (AOI) logic or transmission gates. Assuming complements of all variables are available,

- Draw the static CMOS (AOI) transistor implementation.
- Draw the transmission gate transistor implementation.
- Assume a 50fF load capacitance and ignore all other capacitances. Use all minimum size transistors ($W/L = 0.375 / 0.25$) using the example process of the text. Calculate the worst case delay time for each implementation.

 5. Transmission gate latch:

Draw a transmission gate implementation of a positive latch, i.e. $Q = D$ when $CLK = 1$ and Q latched when $CLK = 0$. Draw the transmission gates at the transistor level and use the inverter symbol for the inverters, i.e.



6. Transmission gate register:

- Draw a transmission gate implementation of a negative edge-triggered register.
- Fill in the timing diagram below.

EE134 Midterm W06

